

Studying the Response of RLC Circuits to Sinusoidal Inputs Using Simulink

R Kwong - kwong@control.utoronto.ca, F Mansouri - farrokh.mansouri@mail.utoronto.ca

• Name:

Lab Date:

• Student No.:

Day of the week:

Time:

• Name:

TA Signature:

• Student No.:

Grade:

1. Natural frequency of an RLC Circuit

1.1 Exercise 1.1

Calculate the natural frequency for the following systems (1 pt)

1. $C = 0.01, L = 0.01$

2. $C = 0.02, L = 0.01$

3. $C = 0.04, L = 0.01$

4. $C = 0.01, L = 0.02$

5. $C = 0.01, L = 0.04$

1.2 Exercise 1.2

- a. Vary the resistance values to show that damping factor increases as you increase the resistance (set $C=0.01$ and $L=0.01$). Deomstrate to TA (TA to check box) (1 pt)

- b. At what resistance does the system transition from underdamped to overdamped? (Keep $L=0.01$ and $C=0.01$) (0.5 pt)

- c. How would underdamped to overdamped transition change if you increase L to 0.02 and C to 0.02? (0.5 pt)

2. RLC circuit response to an external voltage source

2.1 Exercise 2.1

- a. Set the amplitude of your voltage source to 1 and measure the amplitude of the response of the circuit for the following input frequencies. (1 pt)

1. Natural frequency / 5
2. Natural frequency / 2
3. Natural frequency
4. Natural frequency * 2
5. Natural frequency * 5

2.2 Exercise 2.2

Demonstrate the square wave Simulink model and explain peaks in spectrum analyzer. (TA to check box) (1 pt)

3. Applying Fourier Series in circuit analysis

3.1 Exercise 3.1

- a. Use a square wave with 1/32 sec period. Read the frequency of the first 4 peaks on the frequency spectrum, and record the results below. (0.5 pt)

- b. Calculate the first 4 terms of the Fourier series for the square wave using the equation provided, and write down the frequency and amplitude of each term from the Fourier approximation below. (0.5 pt)

- c. Demonstrate the 4-term Fourier series approximation to the square wave. (TA check box) (0.5 pt)

3.2 Exercise 3.2

Compare the response of RLC circuit to the 4-term Fourier series approximation to that of the square wave. (TA check box) (1 pt)

3.3 Exercise 3.3

- a. Demonstrate the 8-term Fourier series approximation to the square wave. (TA check box) (0.5 pt)

- b. Compare the response of RLC circuit to the 8-term Fourier series approximation to that of the square wave. (TA check box) (1pt)

- c. Does the 8-term Fourier series approximate the square wave better, or does the output response with the 8-term Fourier series approximate the output response for the square wave better? (TA check box for explanation) (1pt)